
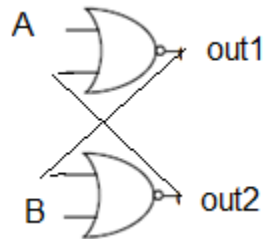


1-How can we make a latch using NOR gates?

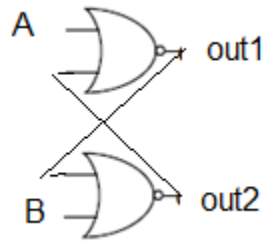
2-If A=B=0 what will happen to this latch?



3- If A=1 and B=0 what will happen to this latch?



4- Right or wrong?

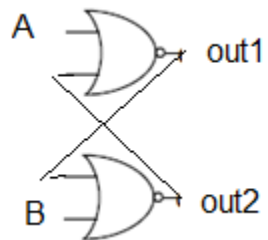

A=RESET and B=SET


5- Explain this Table:

A	B	out1	out2
0	0	Memory	
0	1	1	0
1	0	0	1
1	1	0	0


We don't like A=B=1

6-How can we make a Flip Flop using NOR gates and AND gates?

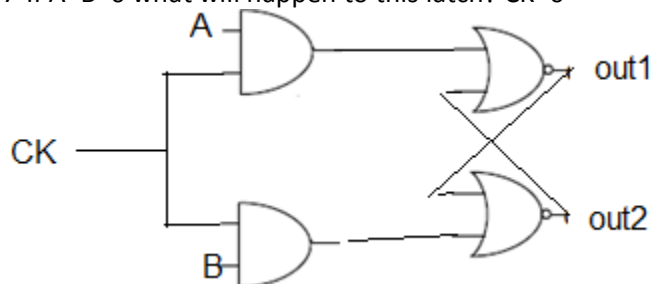
7-If A=B=0 what will happen to this latch? CK=0



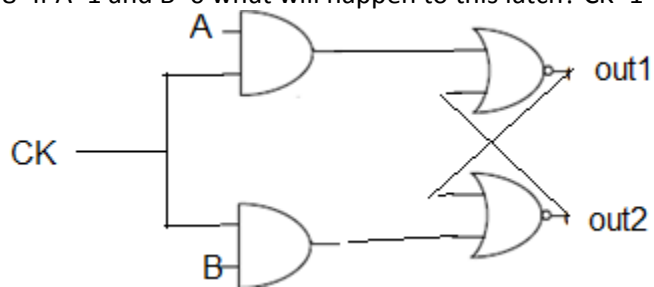8- If A=1 and B=0 what will happen to this latch? CK=1



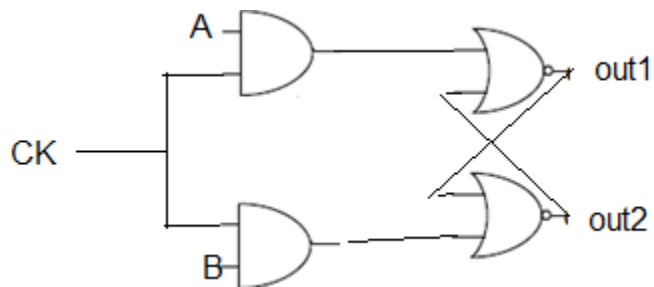
9- Right or wrong? This is a high level triggered RS Flip Flop:



10- Explain this Table: This Truth table belongs to which kind of flip flop?

A	B	Q	Q'
0	0	Memory	
0	1	1	0
1	0	0	1
1	1	Q'	Q

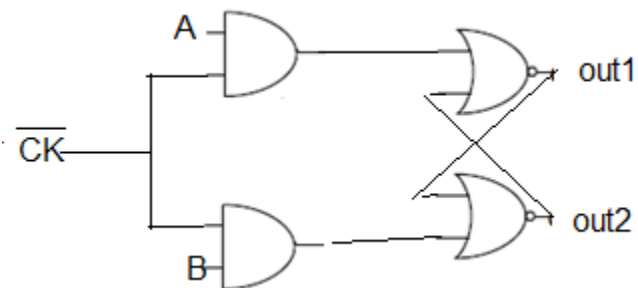11- Right or wrong? This is a high level triggered RS Flip Flop:



12-Design a Rising edge triggered RS flip flop.

13-Design a Falling edge triggered RS flip flop.

14-Why you can't buy a T-Flip Flop?

15- Design a D flip flop.

A) level triggered B) Edge triggered