- 1-What is the truth table of HA<sup>+</sup>?
- 2-What is the truth table of HA?
- 3-What is the truth table of HA<sup>---</sup>?
- 4-This truth table belongs to what?

Α	В	С	S
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	1

5- This truth table belongs to what?

Α	В	С	S	
0	0	1	0	
Ö		1	1	
1	0	1	1	
1	1	Ó	0	

6-This truth table belongs to What?

Α	В	С	S
0	0	-11	1
0	1	0	0
1	0	0	0
1	1	0	1

7-This truth table belongs to what?

Α	В	С	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


8- This truth table belongs to what?

a	b	С	С	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


9-This truth table belongs to what?

a	b	С	С	S
0	0	0	1	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	0
1	0	0	1	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	1

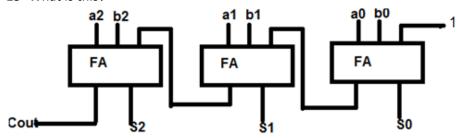
- 10- What is FA<sup>--</sup>
- 11- Does FA<sup>+</sup> Exist?
- 12- Does FA Exist?
- 13- How can we increment the content of a register using FA?
- 14- How can we increment the content of a register using HA?
- 15- What is this?



16- What is this?

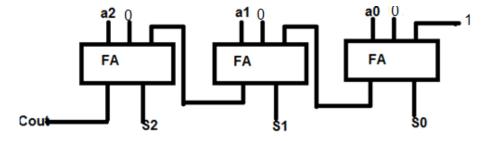

17-What is this?

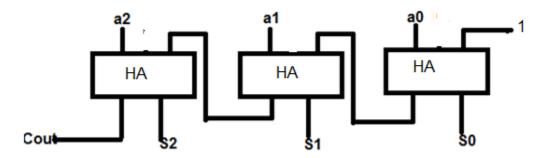

18-If one of the inputs of a full adder is 0 then it will be what?