



# Computer Architecture

Keivan Navi

[Cal Poly Pomona University](#)

[knavi@cpp.edu](mailto:knavi@cpp.edu)

**Office hours: Tu/Th 5:25 Pm to 6:55 Pm**

**Office: 8-49**

# Computer Architecture

Karnaugh Map

K-map

# Karnaugh Map (K-map)

- A Karnaugh map (K-map) is a visual diagram that simplifies Boolean algebra expressions. It's a variation of a truth table that's useful for understanding logic circuits.
- Maurice Karnaugh introduced the K-map in 1953 as an improvement on Edward W. Veitch's 1952 Veitch chart. K-maps are best for functions with two to four variables, but can be used for functions with five or six variables. Using K-maps for functions with seven or more variables is very difficult or impossible.

# K- map (continued)

- To create a K-map, you group adjacent 1's in rows and columns. The rules for K-map groups are:
- Groups must contain only 1's
- Groups must be rectangles
- The sides of the rectangle must be a power of two: 1, 2, or 4
- Every 1 is covered by at least one group
- There are as few groups as possible
- Each group is as large as possible

# Examples of K-map (2 input gates)

- NAND gate:  $(ab)' = \overline{ab}$

	$a'$	$a$
$b'$	1	1
$b$	1	0

- NOR gate :  $(a+b)' = \overline{a+b}$

	$a'$	$a$
$b'$	1	0
$b$	0	0

- b: 

	$a'$	$a$
$b'$	0	0
$b$	1	1

- a XNOR b:  $(a \text{ xor } b)'$

	$a'$	$a$
$b'$	1	0
$b$	0	1

# Examples of K-map (3 input gates)

- 1-  $c'$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	1	1	1
$c$	0	0	0	0

(1)

- 2-  $a'b + bc'$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	0	1	1	0
$c$	0	1	0	0

(2)

- 3-  $(a \text{ xor } b \text{ xor } c)' =$

- 4-  $a'b' + a'c' + b'c' =$

- XNOR  $(a,b,c)$

- Minority  $(a,b,c)$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	0	1	0
$c$	0	1	0	1

(3)

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	1	0	1
$c$	1	0	0	0

(4)

# Example of 3 input K-map (continued)

- 5-  $b'$ :

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	0	0	1
$c$	1	0	0	1

(5)

- 6-  $bc' + ab$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	0	1	1	0
$c$	0	0	1	0

(6)

- 7-  $ab + ac' + bc' = \text{Majority}(a, b, c')$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	0	1	1	1
$c$	0	0	1	0

(7)

# Example of 4 input K-map

- $d'$ :

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd'$	1	1	1	1
$c'd$	0	0	0	0
$cd$	0	0	0	0
$cd'$	1	1	1	1

- $c'd'$ :

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd'$	1	1	1	1
$c'd$	0	0	0	0
$cd$	0	0	0	0
$cd'$	0	0	0	0

- $(a \text{ XNOR } b \text{ XNOR } c \text{ XNOR } d)'$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd'$	1	0	1	0
$c'd$	0	1	0	1
$cd$	1	0	1	0
$cd'$	0	1	0	1

- $a'b' + ab = a \text{ XNOR } b$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd'$	1	0	1	0
$c'd$	1	0	1	0
$cd$	1	0	1	0
$cd'$	1	0	1	0



# Example of 4 input K-map (continued)

- $a'b' + ab + c'd$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	1	1	1
$cd$	1	0	1	0
$cd'$	1	0	1	0

$$a'b'c' + abc = c(a'b' + ab) = c(a \text{ XNOR } b)$$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	0	1	0
$cd$	0	0	0	0
$cd'$	0	0	0	0

- $(a \text{ XOR } b \text{ XOR } c \text{ XOR } d) + bd$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	0	1	1	1
$cd$	1	1	1	0
$cd'$	0	1	0	1

$$(a \text{ XOR } b \text{ XOR } c \text{ XOR } d)'(a+b+c+d)$$

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	0	0	1	0
$c'd$	0	1	0	1
$cd$	1	0	1	0
$cd'$	0	1	0	1

# Sum of Product/ Product of Sum

- **Minterms:** Minterms are the fundamental part of Boolean algebra. Minterm is **the product of N literals where each literal occurs exactly once**. Minterm is represented by m. The output for the minterm functions is 1.
- **Maxterms:** Maxterm is a fundamental part of Boolean algebra. Maxterms are **the sum of various distinct literals in which each literal occurs exactly once**. Maxterm is represented M. The output result of the maxterm function is 0.
- **SOP** uses minterms to create a Boolean expression which is product of Boolean variables whereas **POS** uses maxterms to create a Boolean expression which is sum of Boolean variables.

# Example of minterm

- $abc + a'bc' + de$ :
- In this example  $abc$ , " $a'bc'$ " and  $de$  are minterms
- $ABCD + FGH + HYT'$
- In this example  $ABCD$ ,  $FGH$  and  $HYT'$  are minterms.
- $(a+b)(e+f)$ :
- In this example  $a+b$  and  $e+f$  are Maxterms
- $(yazd + abc' + de)(a+b')(g'+h')$ :
- In this example  $yazd$ ,  $a+b'$  and  $g'+h'$  are Maxterms


# Don't Care (x)

- “Don't care” may also refer to **an unknown value in a multi-valued logic system**, in which case it may also be called an X value or don't know.
- The "Don't care" condition says that **we can use the blank cells of a K-map to make a group of the variables**. To make a group of cells, we can use the "don't care" cells as either 0 or 1, and if required, we can also ignore that cell. We mainly use the "don't care" cell to make a large group of cells.
- **Don't Care cell can be represented by a cross(X) or minus(-) or phi( $\Phi$ ) in K-Maps representing.**

# Examples of Don't Cares

- We have two choices

	a' a	
b'	1	1
b	1	x

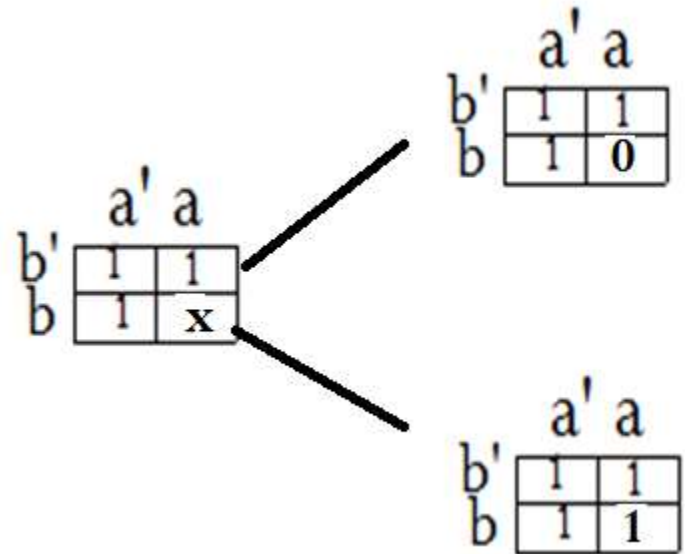

- Which one is a better choice?
- Why?

# Examples of Don't Care (continued)

- We have two choices:

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	x	1	0
$c$	0	1	0	1

- Which one do you chose?

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	0	1	0
$c$	0	1	0	1

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	x	1	0
$c$	0	1	0	1

	$a'b'$	$a'b$	$ab$	$ab'$
$c'$	1	1	1	0
$c$	0	1	0	1

# Examples of Don't Care (continued)

- What is the better choice?

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	x	1	1
$cd$	1	0	1	0
$cd'$	1	0	1	0

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	0	1	1
$cd$	1	0	1	0
$cd'$	1	0	1	0

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	1	1	1
$cd$	1	0	1	0
$cd'$	1	0	1	0

# Examples of Don't Care (continued)

The diagram illustrates four different ways to handle don't care conditions (X's) in a 4-variable Karnaugh map. The central map has X's in the cells corresponding to  $a'b$  and  $ab'$  when  $c'd$ . The four surrounding maps show different simplification strategies:

- Top-left map:** Shows the original map with X's in the  $c'd$  row for  $a'b$  and  $ab'$ .
- Top-right map:** Shows the original map with X's in the  $c'd$  row for  $a'b$  and  $ab'$ .
- Bottom-left map:** Shows the original map with X's in the  $c'd$  row for  $a'b$  and  $ab'$ .
- Bottom-right map:** Shows the original map with X's in the  $c'd$  row for  $a'b$  and  $ab'$ .

The central Karnaugh map is:

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	X	1	X
$cd$	1	0	1	0
$cd'$	1	0	1	0

The four surrounding Karnaugh maps are:

**Top-left map:**

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	0	1	1
$cd$	1	0	1	0
$cd'$	1	0	1	0

**Top-right map:**

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	0	1	0
$cd$	1	0	1	0
$cd'$	1	0	1	0

**Bottom-left map:**

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	1	1	1
$cd$	1	0	1	0
$cd'$	1	0	1	0

**Bottom-right map:**

	$a'b'$	$a'b$	$ab$	$ab'$
$c'd$	1	0	1	0
$c'd$	1	1	1	0
$cd$	1	0	1	0
$cd'$	1	0	1	0